

Total number of printed pages-7

1 (Sem-4) PHY 3

2025

PHYSICS

Paper : PHY0400304


(Analog Electronics)

Full Marks : 45

Time : 2 hours

**The figures in the margin indicate
full marks for the questions.**

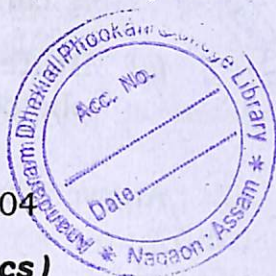1. Answer the following questions : $1 \times 5 = 5$
- (a) What is the output frequency of a full wave rectifier where input frequency is 100Hz?
- (b) In _____ amplifier, the collector current flows for less than half cycle of the input signal.
- (c) What type of amplifier is used to reject hum and static voltage induced into its input leads?



(d) The change in the output wave shape from input wave shape in an amplifier is called _____.

(e) State the biasing method of a photodiode.

2. Answer the following questions : **(any five)**
 $2 \times 5 = 10$

(a) Why does the frequency response of a RC coupled amplifier decrease with increasing frequency after cutoff?

(b) How is electrostatic deflection caused in a CRO?

(c) What happens when the feedback resistance of an operational amplifier is replaced by a (i) capacitor (ii) diode? Write an expression for the output voltage in each case.

(d) Why is a diode called a non-linear device?

(e) Define CMRR. What is the significance?

(f) Explain Q point of a transistor.

(g) What is static and dynamic resistance of a diode?

(h) State the principle behind light emitting diodes.

(i) State the role of coupling capacitors and bypass capacitor in a two stage RC coupled amplifiers.

(j) State the characteristics of an ideal Op-Amp.

3. Answer the following questions : **(any four)**
 $5 \times 4 = 20$

(a) $1 + 2 + 2 = 5$

(i) Draw the circuit diagram of a full wave rectifier circuit with a filter.

(ii) Draw and explain the nature of signal at various stages.

(iii) A power supply A delivers 15V DC with a ripple of $0.6 V_{rms}$ while another power supply B delivers 20V DC with a ripple of $2m V_{rms}$. Which power supply is better and why?

(b) $1 + 1 + 3 = 5$

(i) Define faithful amplification of a transistor amplifier.

(ii) How is faithful amplification obtained in CE configuration?

- (iii) Draw the characteristics of a transistor amplifier and show the active, cutoff and saturation region. Why does these region's occur?

- (c) How does negative feedback effect the input and output impedance of an amplifier? How is the change profitable in practice? 2+3=5

- (d) 2+2+1=5

- (i) What is Barkhausen Criteria for continuous undamped oscillations?

- (ii) How is this criteria met in RC phase-shift oscillator?

- (iii) A phase-shift oscillator uses $10pF$ capacitor. Find the value of R to produce a frequency of $1000kHz$.

- (e) 2+2+1=5

- (i) Draw the characteristic of Zener diode. How does this differ from a normal diode?

- (ii) On what does the breakdown voltage depend on and how can this voltage be changed?

- (iii) How is a Zener diode biased and why?

- (f) Why is CE configuration used in 90-95% of all the transistor applications?

- (g) A sinusoidal signal whose amplitude is $1V$ is applied at the input terminals of

- (i) An inverting amplifier of $R_1 = 1k\Omega$, $R_F = 2k\Omega$.

- (ii) A non-inverting amplifier with $R_1 = 1k\Omega$, $R_F = 2k\Omega$.

- (iii) A comparator circuit.

Draw the output in each case if R_F is the feedback resistance and the power supply is $V_{CC} = \pm 10V$. What is the function of negative feedback from the analysis? 3+2=5

- (h) 1+1+3=5

- (i) What is $3dB$ frequency or half power frequency?

- (ii) What does half power frequency denote?

- (iii) Explain the condition of distortionless amplification based on frequency response.

4. Answer the following questions : (*any one*)

10

(a)

2+3+5=10

- (i) What is stabilization in amplifiers?
- (ii) Why is stabilization required? Explain.
- (iii) Compare stability of Fixed Bias and Voltage Divider bias explaining the reason behind this.

(b)

5+5=10

- (i) How does the energy band diagram of a $P-N$ junction change in forward bias and reverse biased condition?
- (ii) How is the current across the junction caused for the two conditions? Explain with required diagrams.

(c)

2+3+5=10

- (i) What are h parameters?
- (ii) Draw the h parameter equivalent circuit for a CE configuration.
- (iii) Find expressions for input and output impedance of an amplifier as a function of the h parameter.

(d)

2+2+6=10

- (i) Define Slew Rate of an OP-AMP.
- (ii) What is the use of slew rate in applications of OP-AMPs?

(iii) It is required to design a circuit using OP-AMP to obtain the output

$$V_{out} = (2V_1 + 3V_2 - 4V_3)$$

draw a circuit to obtain the output if V_1 , V_2 and V_3 are the inputs.